

وَقُلْ رَبِّ زِدْنِي عِلْمًا

---

Analog CMOS IC Design training @ ITI

Under supervision of Dr.Hesham omran

---

Lab 11 (Mini Project 02)

Fully-Differential Folded Cascode OTA + CMFB circuit

Tools : Analog Designer's Toolbox (ADT) + Cadence


Mohamed nasser

---


ECE Senior 1 Student @ ASU

# Gm/id Methodology


## □ Pmos

 


GM/ID 15 L 3u ft 12.61MEG

 

GM/ID 15 L 3u vgs 836.9m

 

GM/ID 15 L 3u w/id 21.7

 

GM/ID 15 L 3u ft 12.61MEG

LUT Settings

LUT: pmos\_03v3

Corner: TT

Temp (°C): 27.0

Frequency: 1

Stack: 1

ID: 10u

gm/ID: 5:25

L: min,1u:1u:5u

VDS: 0.5

VSB: 0

Results:


Name	Value
1 ID	Plot
2 IG	Plot
3 L	Plot

Y-Expr: ft


Plot Append

# Gm/id Methodology


## Nmos

 


GM/ID 15 L 3u vgs 711.2m

 

GM/ID 15 L 3u w/id 5.175

 

GM/ID 15 L 3u ft 60.3MEG

 

GM/ID 15 L 3u VA 37

Import: Plot 1A OK

LUT Settings

LUT: nmos\_03v3

Corner: TT

Temp (°C): 27.0

Frequency: 1

Stack: 1

ID: 10u

gm/ID: 5:25

L: min,1u:1u:5u

VDS: 0.5

VSB: 0


Results:

Name	Value
1 ID	Plot
2 IG	Plot
3 L	Plot


Y-Expr: ft

Plot Replace

# Folded+ CMFB network

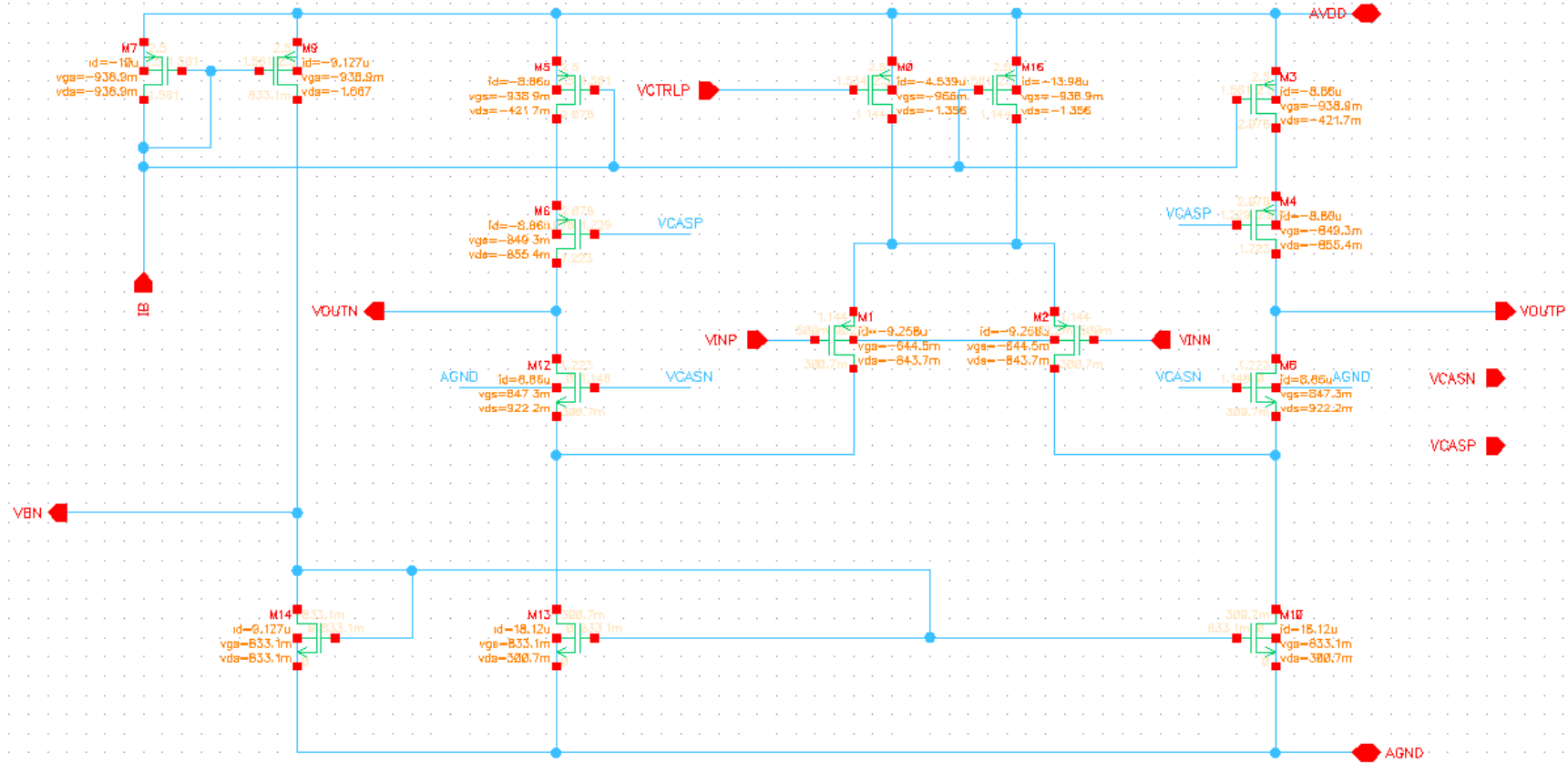

# Folded+ CMFB network

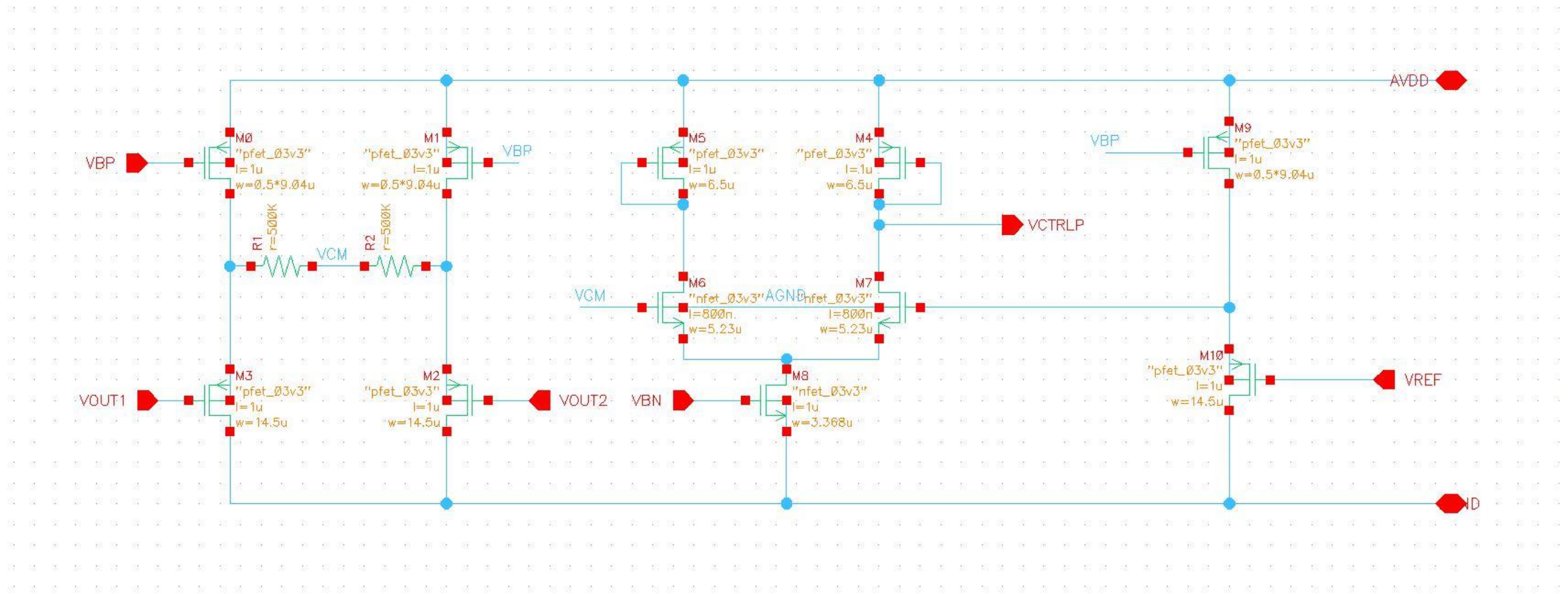

# Hand Analysis

□ Settling time spec:

$$ts = \frac{4.6}{t} = \frac{4.6}{Bwcl} \Rightarrow Bwcl = \frac{4.5}{100n} = 46M \frac{rad}{sec} = \mathbf{7.3M\ hz}$$

$$GBW = Wu = Acl * BWcl = 2 * Bwcl = 90M \frac{rad}{sec} = \mathbf{14.6\ Mhz}$$

$$GBW = \frac{gm(ip)}{cout} = \frac{gm(ip)}{Cl + Cf(1 - B)} = \frac{gm(ip)}{Cl + \frac{3}{4}Cf} \Rightarrow gm(ip) = 130\ us, \text{ let } gm = 160\ us$$

$$\text{assuming } \frac{gm}{id} = 20 \text{ for in. pairs} \Rightarrow \mathbf{IB1 = 9u} \text{ "to get margin and self loading"}$$

□ Dc open loop gain and CL gain specs:

$$LG = \frac{Vout}{If} * Aol(R) = \frac{Vout}{VfB} * Aol = \frac{Cf}{Cf + Cs + cself} * Aol = \frac{1}{4} * Aol \geq 60dB \Rightarrow \mathbf{Aol \geq 73\ dB}$$

□ From phase margin spec:

$$PMcl = 90 - \arctan\left(\frac{wucl}{wpnd}\right) \geq 70 \Rightarrow Wpnd = 3 Wucl$$

$$\text{we know that } GX = \frac{1}{4} Wucl \Rightarrow GX = Wpnd \Rightarrow \mathbf{PMol \geq 37}$$

# Hand Analysis

□ we will use split ratio = 1

$$IB2 = IB1 = 9u$$

□ assuming  $\frac{gm}{id}$  and  $L$  as a first step to make the design easier:

□ Using charts ::

- input pairs:  $\frac{gm}{id} = 20, l = 400n \Rightarrow w = 85u$
- current source devices (nmos) :  $\frac{gm}{id} = 10, L = 1u \Rightarrow w = 8.25u$
- current source devices(pmos):  $\frac{gm}{id} = 10, l = 1u \Rightarrow w = 18u$
- cascode devices :  $\frac{gm}{id} = 15, L = 500n \Rightarrow w = 25u$  pmos & 7 u nmos

# Hand Analysis

$$\square V_{cacp} \leq V_{DD} - V_{GS}(5) - V * (4)$$

$$V_{GS}(4) = 848.7m$$

$$V * (5) = \frac{2}{\frac{gm}{id}} = 200 \text{ mv}$$

$$\mathbf{V_{casp} \leq 1.45 \text{ V}}$$

$$\square V_{casn} = V_{GS}(3) + V * (2)$$

$$V * (2) = \frac{2}{\frac{gm}{id}} = 200 \text{ mv}$$

$$V_{GS}(3) \Rightarrow \text{From ADT} = 752.3m$$

$$\mathbf{V_{casn} \geq 960 \text{ mv}}$$

□ CMIR range :

$$CMIR_{high}: V_{DD} - V * (6) - V_{in} \geq V_{th}(1)$$

$$V_{th}(1) = 750 \text{ mv}, V * (6) = 200 \text{ mv}$$

$$V_{in} \leq 1.55 \text{ v}$$

$$CMIR_{LOW}: V_{casn} - V_{GS}(3) - v * (3) - v_{in} \leq V_{th}(1)$$

$$V_{th}(1) = 750 \text{ mv}, V * (3) 140 \text{ mv}, V_{GS}(3) = 752 \text{ mv}, \mathbf{\text{let } V_{casn} = 1.1 \text{ v}}$$

$$\mathbf{v_{in} \geq -0.54 \text{ mv}}$$



# cockpit


## □ Getting accurate sizing from cockpit adt

Design Variable	Value	Output Variable	Nominal
M1a(ID)	9u	VCASCP	1.229
M1a(L)	400n	VBP	1.559
M2a(L)	1u	VCMFB	1.558
M3a(L)	500n	VINP	500m
M4a(L)	500n	VINN	500m
M5a(L)	1u	M1a(W)	84.63u
M6(L)	1u	M2a(W)	8.423u
M1a(GM/ID)	20	M3a(W)	6.778u
M2a(GM/ID)	10	M4a(W)	23.53u
M3a(GM/ID)	15	M5a(W)	18.08u
M4a(GM/ID)	15	M6(W)	34.85u
M5a(GM/ID)	10	MVBN(W)	8.423u
M6(GM/ID)	10	MVBP(W)	18.08u
VDD[Nominal]	2.5	MVCMFB(W)	34.85u

Design Variable	Value	Output Variable	Nominal
M1a(ID)	9u	DC Gain	10.78k
M1a(L)	400n	BW	5.041k
M2a(L)	1u	GBW	54.37MEG
M3a(L)	500n	UGF	54.12MEG
M4a(L)	500n	PM	77.81
M5a(L)	1u	Total Input ...	79.83u
M6(L)	1u	Thermal Inpu...	383.1a
M1a(GM/ID)	20	Input Referre...	3.034m
M2a(GM/ID)	10	Area	247.2p
M3a(GM/ID)	15	Cgg	123.2f
M4a(GM/ID)	15	Itotal	36u
M5a(GM/ID)	10	VDD	2.5
M6(GM/ID)	10	VIN_CM	500m
VDD[Nominal]	2.5	VOUT_CM	1.25

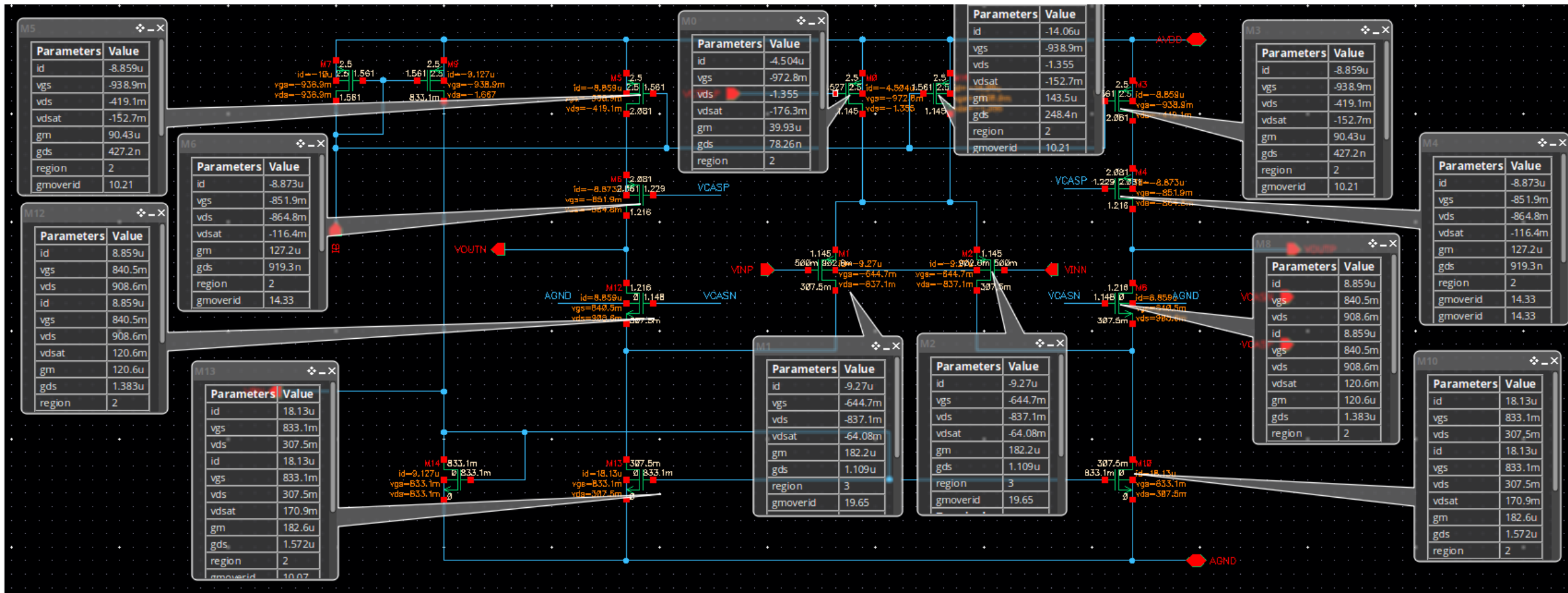
# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

- ❑ Schematic of the OTA and bias circuit with DC node voltages and transistors OP parameters



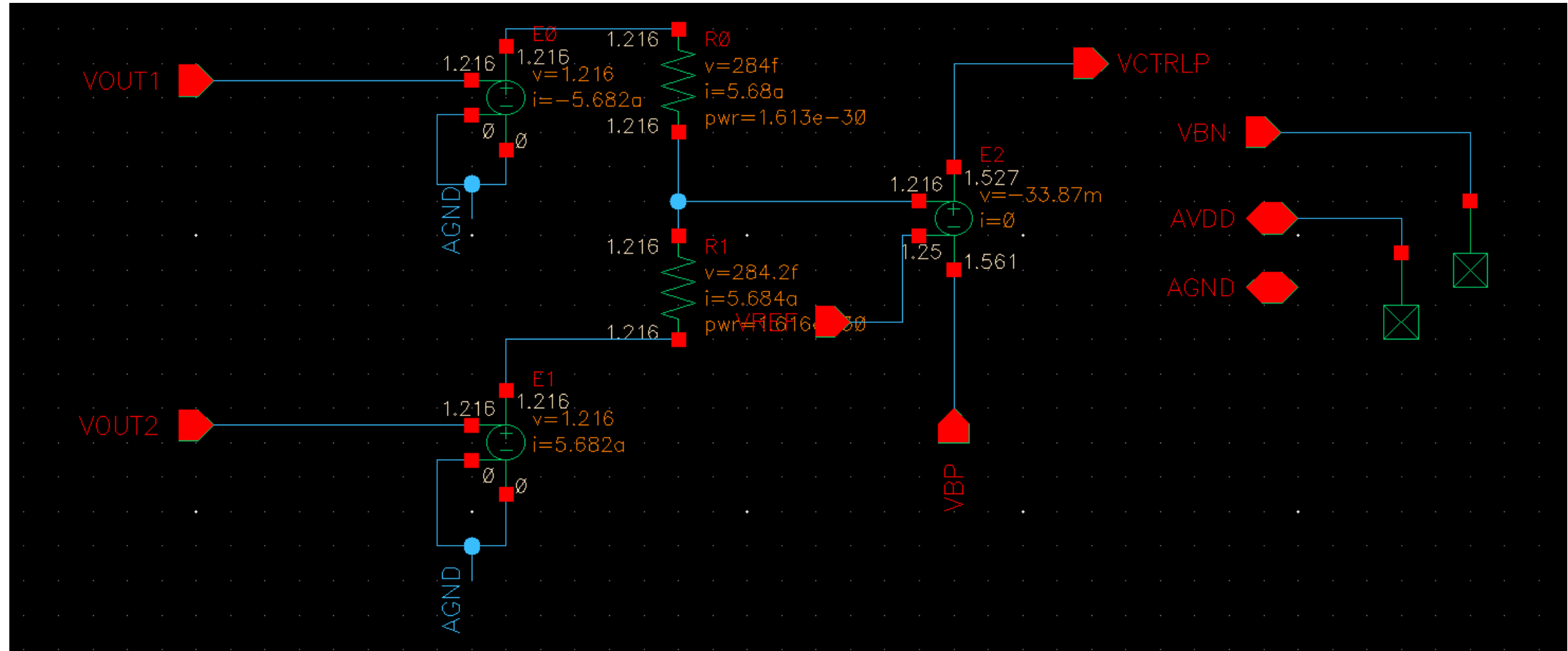
# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

- ❑ Schematic of the OTA and bias circuit with DC node voltages and transistors OP parameters


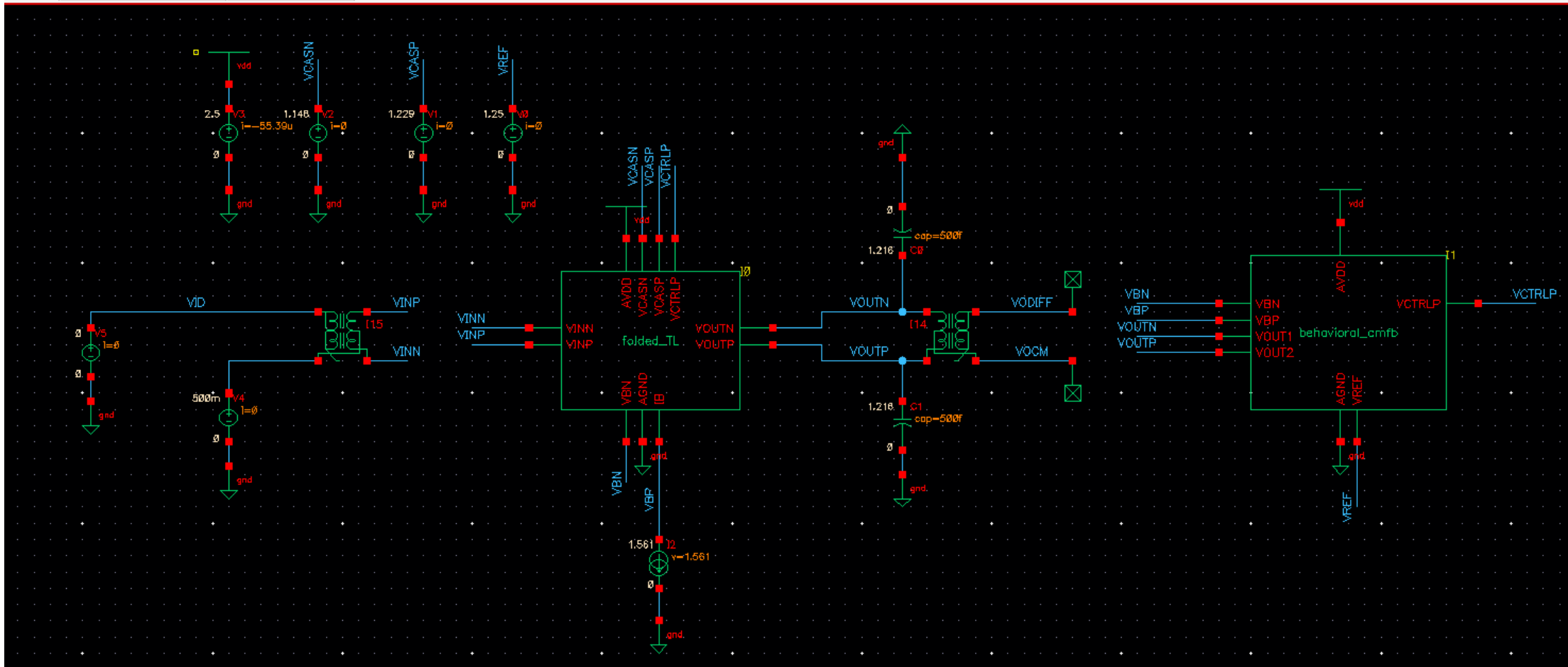
# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

- ❑ Schematic of the OTA and bias circuit with DC node voltages and transistors OP parameters



# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

❑ What is the CM level at the OTA output?

➤  $V_{ocm} = 1.22\text{ v}$

❑ What are the differential input and output voltages of the error amplifier? What is the relation between them?

➤  $diff\ input = 0.027\text{ v}$  ,  $diff\ output = 0.027$  ,  $A_{cmfb} = 1$

# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

□ Diff small signal ccs

□ Plot diff gain (magnitude in dB and phase) vs frequency.


dB20(mag(v("/VODIFF" ?result

Fri Sep 6 18:38:50

1

... (v("/VODIFF" ?result "ac"))

...208dB 0.00011

 



# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

□ phase vs frequency


phase(v("/VODIFF" ?result

Name

■ ... (v("/VODIFF" ?result "ac"))

Fri Sep 6 18:38:50

1

 

# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

❑ Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab11:tb_part3:1	phase(v("/MODIFF" ?result "ac"))				
lab11:tb_part3:1	AO	6.7k			
lab11:tb_part3:1	AO_dB	76.52			
lab11:tb_part3:1	dB20(mag(v("/MODIFF" ?result "...				
lab11:tb_part3:1	GBW	56.3M			
lab11:tb_part3:1	UGF	55.77M			
lab11:tb_part3:1	BW	8.383k			
lab11:tb_part3:1	dB20(phase(v("/MODIFF" ?result ...				
lab11:tb_part3:1	phaseMargin(VF("/MODIFF"))	-106.9			
lab11:tb_part3:1	(phaseMargin(VF("/MODIFF")) + 1...	73.12			




# PART 3: Open-Loop OTA Simulation (Behavioral CMFB)

❑ Compare simulation results with hand calculations in a table (use SS parameters from OP simulation in your hand analysis) indices is from cockpit 456 M 41M 37.75

$$GBW = \frac{gm1}{cout} = \frac{gm1}{2\pi(cl + Cself_{ota})} = \frac{182\mu s}{0.5p + 50f} \approx 52 \text{ Mhz}$$

$$Aol = G_M R_{out} = gm1 * (((gm4 + gmb4) * r_{o4} * r_{o5}) || ((gm3 + gmb3) * r_{o3} * (r_{o2} || r_{o1}))) = 182\mu s ( (179\mu * \frac{1}{919n} * \frac{1}{427n}) || (152\mu s * \frac{1}{1.383u} * (1/1.57\mu || 1/1.1\mu)) \approx 6825$$
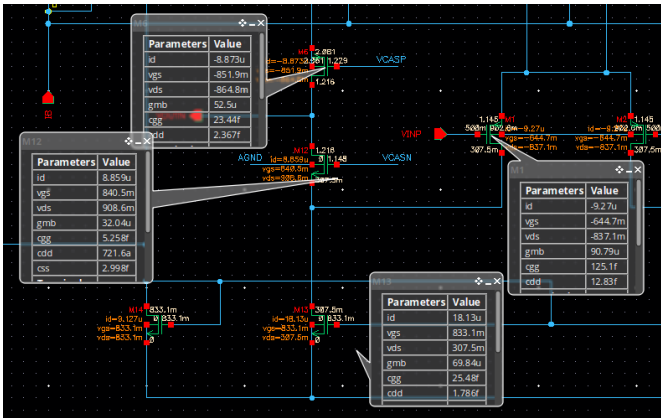
$$BW = \frac{1}{2\pi * (Cl + c_{self}) * Rout} \approx 7.7 \text{ khz}$$



	Simulation	Hand analysis
Ao	6700	6825
GBW	56 Mhz	52 Mhz
BW	8.4 K	7.7 k

# PART 4: Open-Loop OTA Simulation (Actual CMFB)

## ❑ CMFB design :

### ➤ *error amplifier*

- *Pmos DC is same as MX adjusting 20% of current*
- *Input Nmos  $\Rightarrow gm/id = 20, l = 500n, i = 7.2u/2, \Rightarrow W = 13u$*
- *Tail CS  $\Rightarrow$  supply  $0.4 i_{tail}$  of folded ( $W * 0.4$ )*

### ➤ *CD $\Rightarrow$ to avoid loading*

- *Pmos cs supply 0.25 Current supplied By M5 in folded  $W5 * 0.25$*
- *Pmos input :  $l = 1u, i = 9u/4, gm/id = 15 \Rightarrow w = 14.5u$*


### ➤ *Vref value :*

- *Best Vref value = 950 mv Maximizing swing  $2v * \Rightarrow 1.5 (VDD - |VGSP| + V * p)$*

## ❑ *Total current consumption = 14u < 50% of folded*

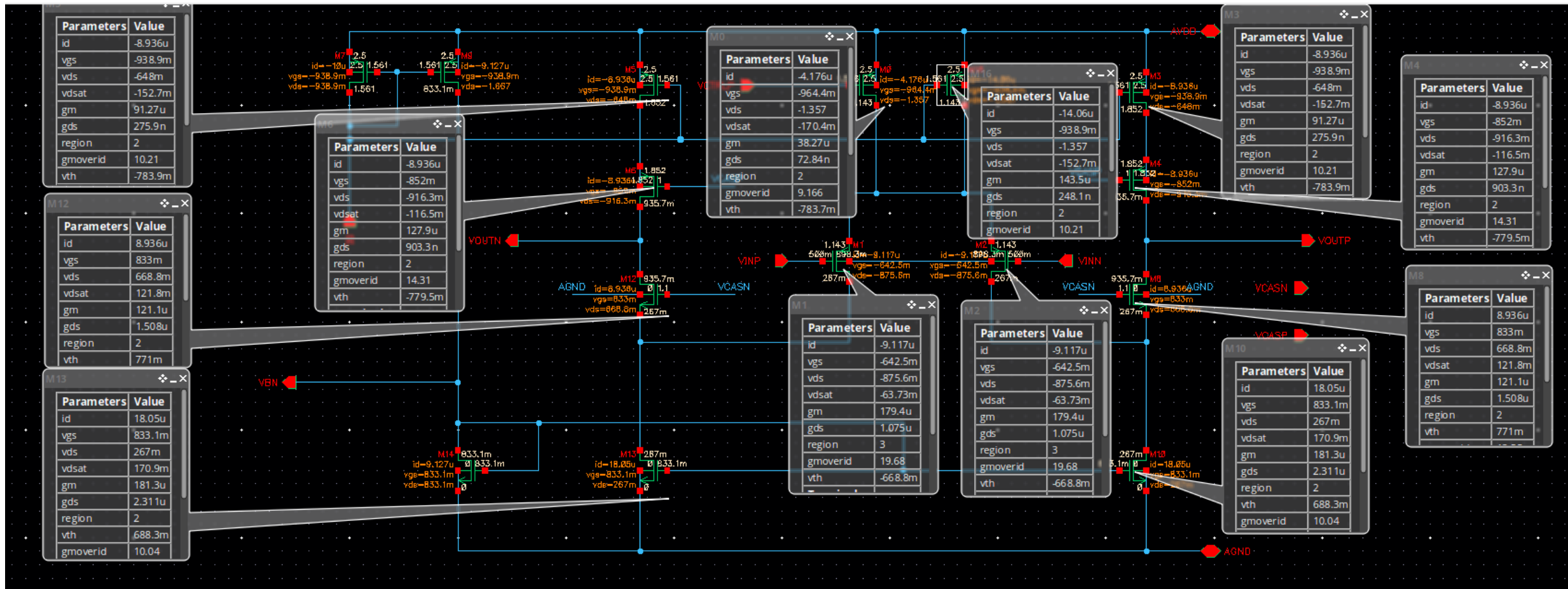
## PART 4: Open-Loop OTA Simulation (Actual CMFB)

- ❑ Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters



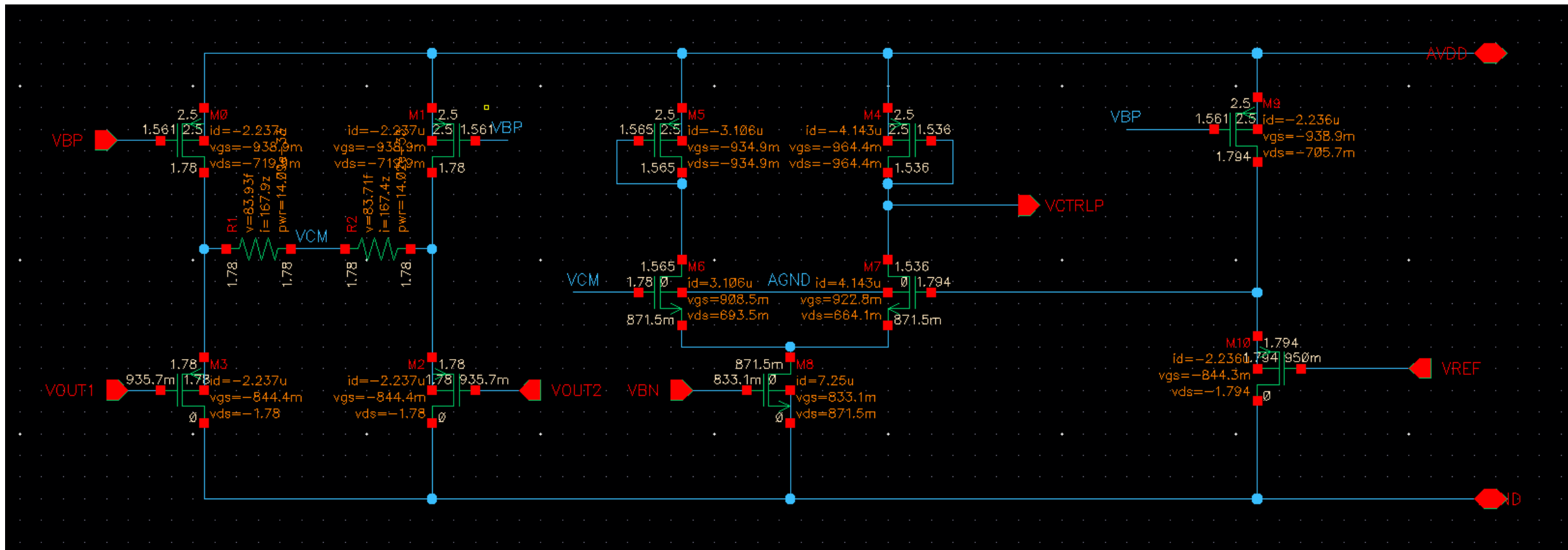
# PART 4: Open-Loop OTA Simulation (Actual CMFB)

- ❑ Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters


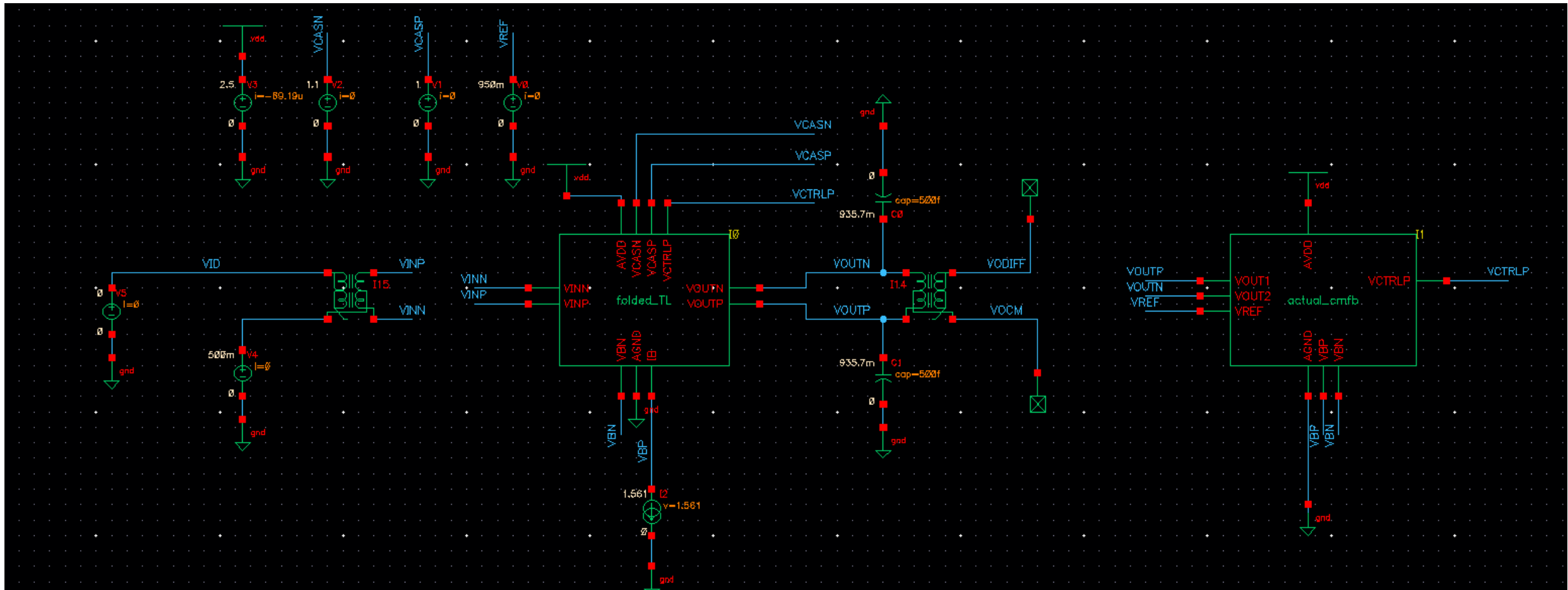
# PART 4: Open-Loop OTA Simulation (Actual CMFB)

- ❑ Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters



# PART 4: Open-Loop OTA Simulation (Actual CMFB)

❑ What is the CM level at the OTA output? Why?

➤  *$\approx 936\text{ mV}$  as the cmfb network adjust M6 current to maintain the  $v_{ocm}$  near to  $\approx v_{ref}$  but as Mx in error amplifier and M6 in folded has different  $V_{ds}$  it will be hard to have error = 0*

❑ What are the differential input and output voltages of the error amplifier? What is the relation between them?

➤ *diff input = 0.014 , difoutput = 0.029 ,  $A_{cmfb} \approx 2$  "Gain of error amplifier"*

# PART 4: Open-Loop OTA Simulation (Actual CMFB)

□ Diff small signal ccs

□ Plot diff gain (magnitude in dB and phase) vs frequency.


dB20(mag(v("/VODIFF" ?result

Fri Sep 6 19:59:09

1

...2395dB ...5


...

 


 
# PART 4: Open-Loop OTA Simulation (Actual CMFB)



□ phase vs frequency





# PART 4: Open-Loop OTA Simulation (Actual CMFB)


❑ Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab11:tb_part4:1	phase(v("/VODIFF" ?result "ac"))				
lab11:tb_part4:1	Ao	5.152k			
lab11:tb_part4:1	A0_dB	74.24			
lab11:tb_part4:1	GBW	54.7M			
lab11:tb_part4:1	UGF	53.98M			
lab11:tb_part4:1	BW	10.59k			
lab11:tb_part4:1	dB20(mag(v("/VODIFF" ?result "...				
lab11:tb_part4:1	PM	-106.7			
lab11:tb_part4:1	(PM + 180)	73.3			



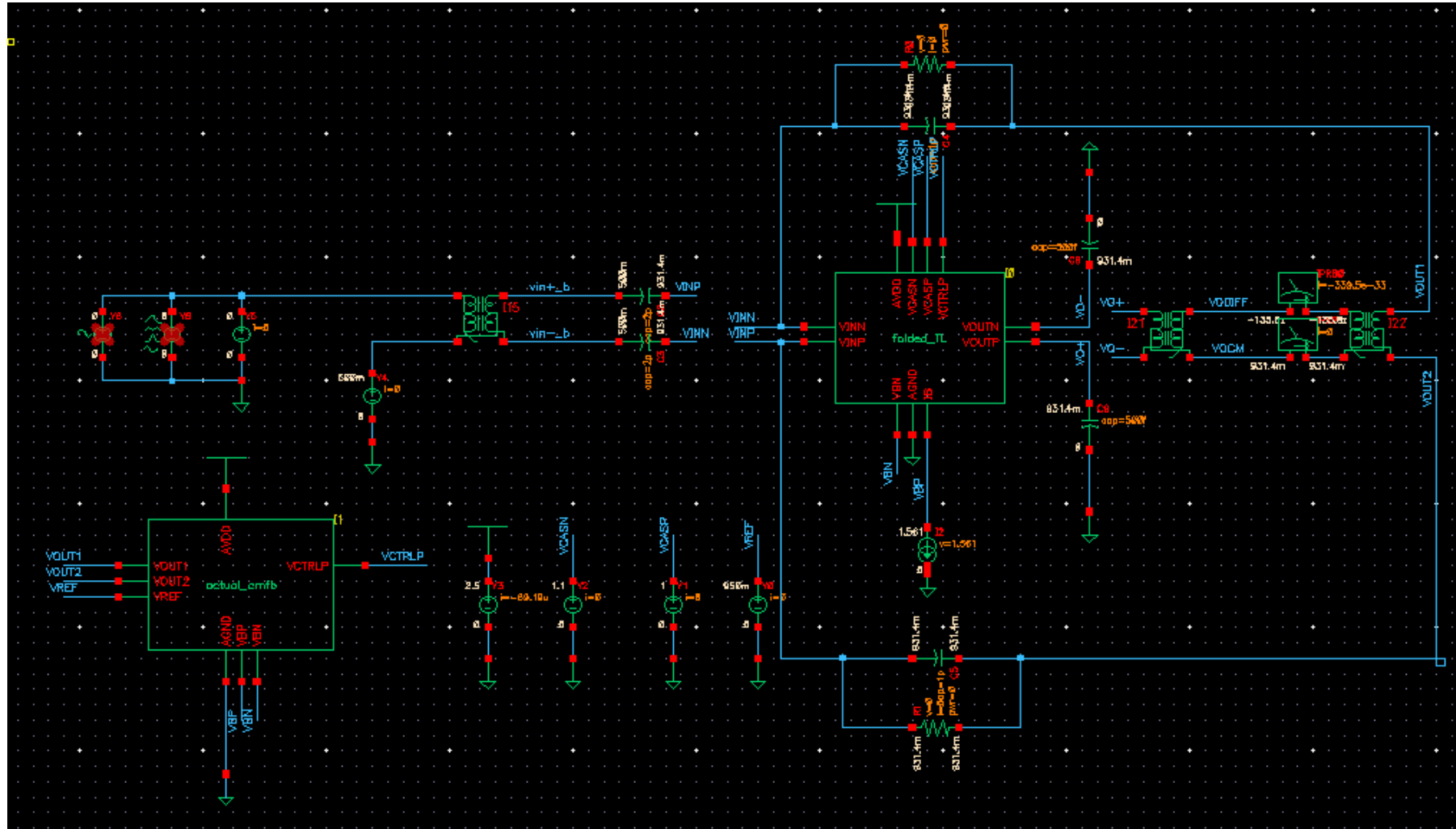
# PART 5: Closed Loop Simulation (AC and STB Analysis)

- ❑ Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters


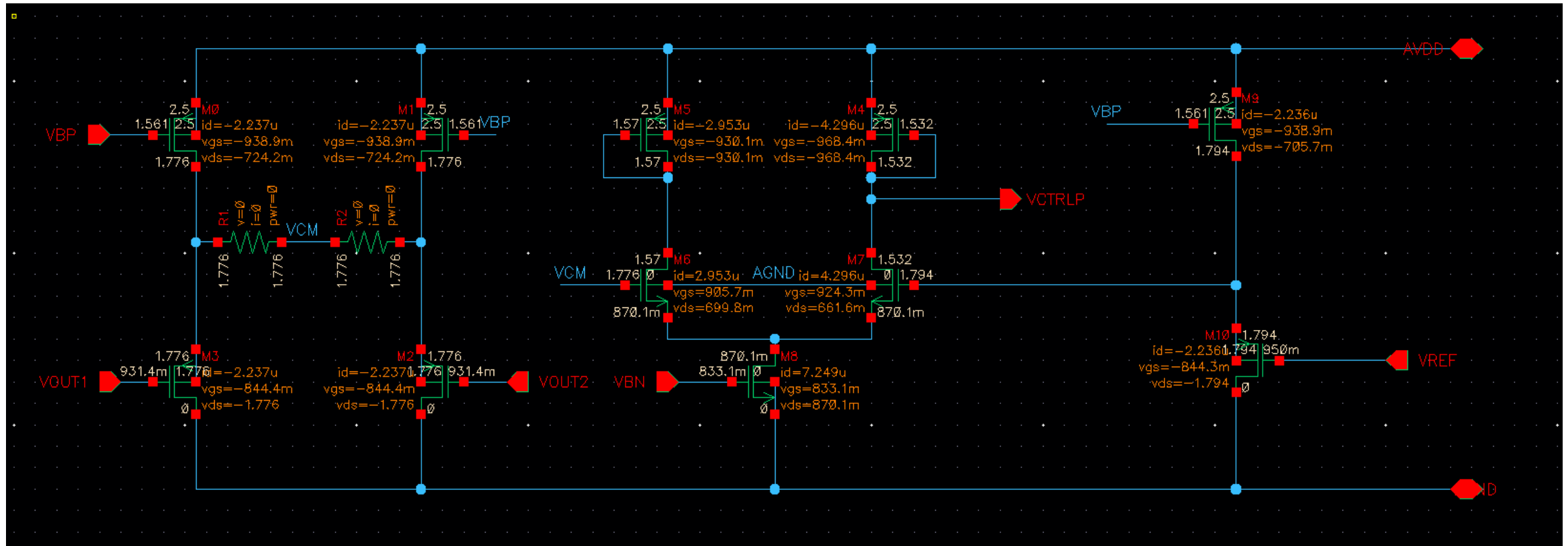
# PART 5: Closed Loop Simulation (AC and STB Analysis)

- ❑ Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters



# PART 5: Closed Loop Simulation (AC and STB Analysis)

- ❑ What is the CM level at the OTA output? Why?
  - $932\text{ mV}$ , as the cmfb network works at making  $v_{ocm} = v_{ref}$ , but the apparent error is due to the low gain of error gain
  
- ❑ What is the CM level at the OTA input? Why?
  - $932\text{ mV} = V_{ocm}$ , in dc  $C_{in}$  is O.C, the cmfb adjust  $V_{ocm}$  and  $V_{ocm}$  adjust due to small dc res. we used, @ low freq it is unity feed back but flipped!

# PART 5: Closed Loop Simulation (AC and STB Analysis)

## □ Plot VODIFF vs frequency


AC Analysis `ac`: freq = (1 Hz -> 10 GHz)

Name

■ /VODIFF



0

 

# PART 5: Closed Loop Simulation (AC and STB Analysis)


- ❑ Use Measures or cursors to calculate circuit parameters (DC gain, CL BW, CL GBW)

lab11:part5_tb:1	Acl	1.999			
lab11:part5_tb:1	GBW_cl	17.71M	> 14.4M		pass
lab11:part5_tb:1	BW_cl	8.95M	> 7.16M		pass


 
# PART 5: Closed Loop Simulation (AC and STB Analysis)


- Plot loop gain in dB and phase vs frequency for the two simulations overlaid. Diff loop has higher gain





 
# PART 5: Closed Loop Simulation (AC and STB Analysis)


□ phase vs frequency for the two simulations overlaid.



# PART 5: Closed Loop Simulation (AC and STB Analysis)

- ❑ Compare GBW and PM of diff and CM loops. Comment.

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab11:part5_tb:1	cmfb_LG_PM	83.84			
lab11:part5_tb:1	cmfb_LG				
lab11:part5_tb:1	cmfb_GBW_LG	2.323M			
lab11:part5_tb:1	cmfb_DC loop gain	722.6			

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab11:part5_tb:1	diff_LG_PM	87.82			
lab11:part5_tb:1	diff_LG				
lab11:part5_tb:1	diff_GBW_LG	7.381M			
lab11:part5_tb:1	diff_DC loop gain	1.44k			

- ❑ *PM of diff loop is higher  $\Rightarrow$  More stable*

- ❑  $BW_{cmfb} = \frac{GBW_{cmfb}}{DC\ gain\_cmfb} = 3215hz$

$$BW_{diff} = \frac{GBW_{diff}}{DC\ gain\_diff} = 5125$$

$$t_{diff} = 0.62\ t_{cmfb} \Rightarrow \text{diff loop is faster}$$

# PART 5: Closed Loop Simulation (AC and STB Analysis)

- ❑ Compare DC LG and GBW of the diff loop with those obtained from open-loop simulation. Comment

	Open loop (B=1)	LG IN Closed loop(B=1/5)
Dc loop gain	6.7 K	1.4K
GBW	54 Mhz	7.4 M hz

- ❑ *Closing the loop gives us*

- $c_{out} = C_l + C_f(1 - B)$  ↑↑ GBW ↓↓


- $LG = B * A_{ol} \Rightarrow B = \frac{C_f}{C_f + C_s + c_{self}} = \frac{1}{4}$

- $G_X = B * GBW_{ol}$

- ❑ Closing the loop decreased the GBW and DC loop gain.
 
# PART 6: Closed Loop Simulation (Transient Analysis)

□ Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOVM overlaid



# PART 6: Closed Loop Simulation (Transient Analysis)

- ☐ Do you notice any differential/CM ringing? Are both loops stable with adequate PM?
- No , just coupling , yes both are stable with adequate PM.
- ☐ Calculate the 1% settling time and compare it to the required specification.


Test	Output	Nominal	Spec	Weight	Pass/Fail
lab11:part5_tb:1	/vin+_b	✓			
lab11:part5_tb:1	/vin-_b	✓			
lab11:part5_tb:1	/VO-	✓			
lab11:part5_tb:1	/VO+	✓			
lab11:part5_tb:1	/VOCM	✓			
lab11:part5_tb:1	riseTime(v("/VODIFF" ?result "tr...	94.89n			

	spec	achieved
Rise time	100n	94n

- ☐ If the specification **was not satisfied** , what design changes could be a possible solution? Increase gm of input pair
 
# PART 6: Closed Loop Simulation (Transient Analysis)

□ Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOVM overlaid






# PART 6: Closed Loop Simulation (Transient Analysis)

---

- ☐ Do you notice any differential/CM ringing? Are both loops stable with adequate PM?
- No , just coupling , yes both are stable with adequate PM.
 
# PART 6: Closed Loop Simulation (Transient Analysis)



□ Plot the transient signals at VIDIFF and VODIFF overlaid in the same figure.





# PART 6: Closed Loop Simulation (Transient Analysis)

❑ Calculate the diff input and output peak-to-peak swings and the closed loop gain.

lab11:part5_tb:1	vid				
lab11:part5_tb:1	vod				
lab11:part5_tb:1	pp_vod		599.5m		
lab11:part5_tb:1	pp_vid		300m		
lab11:part5_tb:1	clgain		1.999		

# PART 6: Closed Loop Simulation (Transient Analysis)

## □ Swing spec

